



Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer

Page No : 1 of 23

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept



Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer


Page No : 2 of 23

- 1 a) i) Cycle : “ In a sinusoidal AC waveform each repetition consisting of one positive and one identical negative part is called as one cycle of the waveform.” 1 mark  
ii) Time period : “ Time period is defined as time in seconds for waveform of an AC quantity to complete one cycle. 1 mark


- 1 b) Given expression is,  $i = 10 \sin (100 \Pi t)$   
Comparing it with,  $I = I_m \sin (2 \Pi f_0 t)$   
we get,  $I_m = 10$ ,  $2 \Pi f_0 = 100 \Pi$   
i) To calculate frequency:  $2 \Pi f_0 = 100 \Pi$   
 $\therefore 2 f_0 = 100$   
 $\therefore f_0 = 50 \text{ Hz}$  1 mark

- ii) To calculate  $I_{\text{rms}}$ :  $I_{\text{rms}} = 0.707 I_m$   
 $\therefore I_{\text{rms}} = 0.707 \times 10 = 7.07 \text{ A}$  1 mark

- 1 c) Definition: **Power factor** is defined as the ratio of true power and apparent power of an AC circuit. 1 mark  
In case of R-L series circuit, power factor is lagging due to negative sign of  $\Phi$ . 1 mark

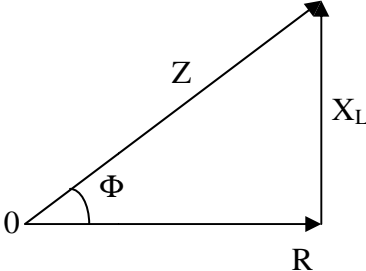- 1 d)  1 mark  
Labeled 2marks,  
unlabeled

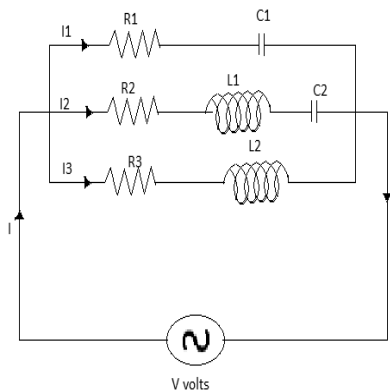- 1 e) A parallel circuit has two or more series circuits connected parallel with each other across a common pair of nodes as shown in figure. The total current flowing into the parallel combination gets divided in inverse proportion to the impedance value. 1 mark





**Summer – 2014 Examinations**

**Subject Code : 17323 (ECN)**


**Model Answer**

**Page No : 3 of 23**

1 f) There are two components of admittance:

- i) Conductance(G): It is ratio of resistance(R) and squared impedance( $Z^2$ ) 1 mark
- ii) Susceptance(B): It is ratio of reactance(X) and squared impedance( $Z^2$ ) 1 mark

1 g)

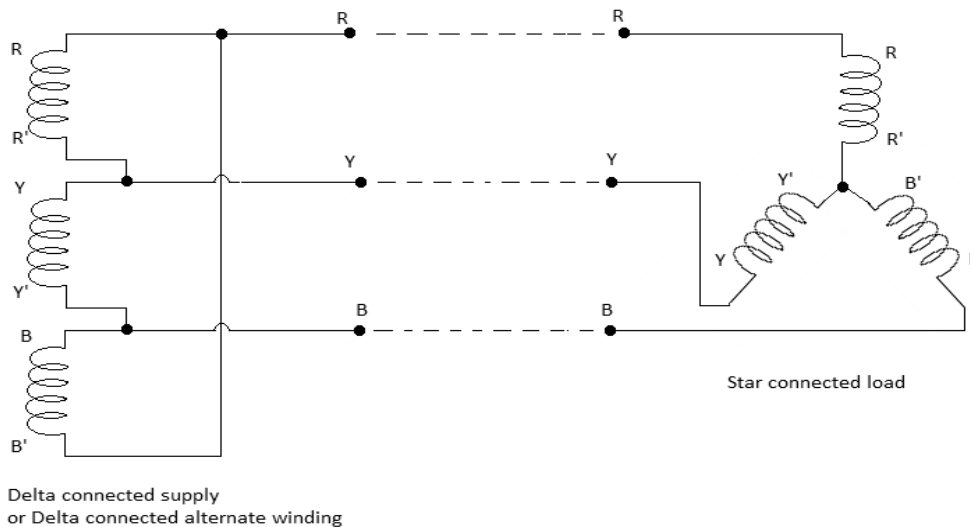

Labeled 2  
marks,  
unlabeled  
1 mark


The delta connected windings of the supply side may belong to the sources or to the secondary of the transformer.

1 h) The mathematical equation for three phase voltages displaced by  $120^\circ$  is given by,

$$\begin{aligned} V_R &= V_m \sin \omega t && \text{1 mark} \\ V_Y &= V_m \sin (\omega t - 120^\circ) && \text{1 mark} \\ V_B &= V_m \sin (\omega t - 240^\circ) \end{aligned}$$

1 i) Steps to transform Voltage source to Current source:

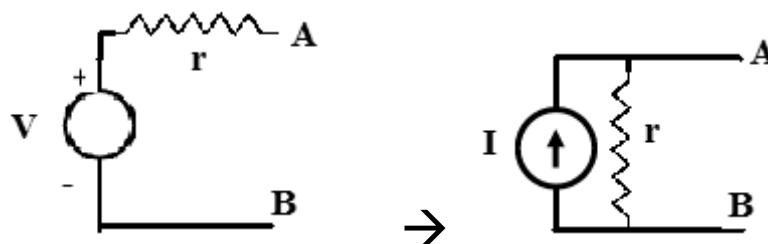- 1) Calculate equivalent current source as the short circuit current through the voltage source terminals: ( $I = V / r$ ) 1 mark
- 2) The Shunt Resistance of current source: ( $R_{sh} = r$ )
- 3) Draw the equivalent source.



1 mark

1 j) Statement of Maximum Power transfer Theorem (for DC circuits):

“It states that, the maximum amount of power is delivered to the load resistance when the load resistance is equal to the Thevenin’s equivalent source resistance of the



network supplying the power across the load terminals.”

According to this theorem, condition for maximum power to be transferred is,  $R_L = R_{TH}$ , where  $R_{TH}$  = Thevenin’s source resistance across  $R_L$ . 2 marks

1 k) Statement of Thevenin’s Theorem :


It states that current flowing through any resistance (referred as load resistance  $R_L$ ) of an active, bilateral circuit can be calculated by Thevenin’s theorem as

$$I_L = V_{th} / (R_{th} + R_L) \quad 1 \text{ mark}$$

where,

$V_{th}$  = the open circuit voltage measured across load terminals by removing the load resistance

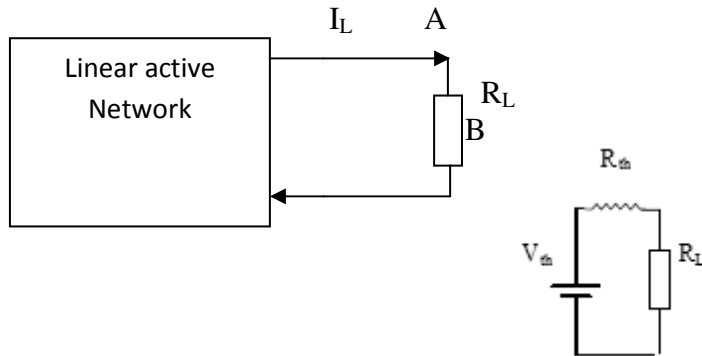$R_{th}$  = the Thevenin’s equivalent resistance measured across load terminals by removing the load resistance and replacing all sources by their internal resistances



- 1 l) i) At the instant of switching (sudden or abrupt change in circuit condition), inductor (L) opposes the change in current in it and behaves as open circuit. 1 mark
- ii) At the instant of switching (sudden or abrupt change in circuit condition), capacitor (C) opposes change in voltage across it and behaves as short circuit. 1 mark

2 a) Given equation is,  $e = 25 \sin (314 t)$

Comparing it with  $e = V_m \sin(\omega t)$

Amplitude  $V_M = 25 \text{ V}$  1 mark

RMS value = peak value/ $\sqrt{2} = 25/\sqrt{2} = 17.67 \text{ V}$ . 1 mark

Frequency =  $\omega/2\pi = 314/2\pi = 50 \text{ Hz}$ . 1 mark

Time period =  $1/\text{frequency} = 1/50 = 0.02 \text{ sec}$  1 mark




**Summer – 2014 Examinations**

**Subject Code : 17323 (ECN)**

**Model Answer**

**Page No : 5 of 23**

2 b)

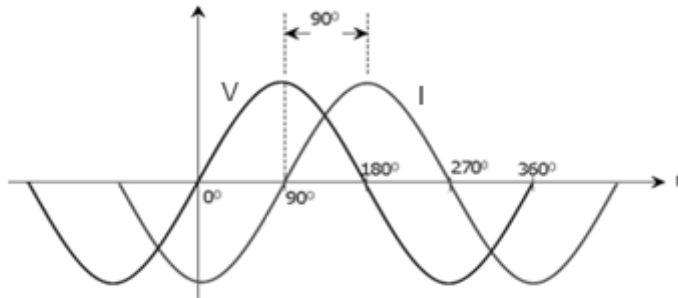

1 mark

Fig. Waveform of voltage and current for purely inductive circuit.

Expression for supply voltage can be given by,  $v = V_m \sin \omega t$

Now, Current in purely inductive circuit is,  $I = (1/L) \int v dt$

$$\therefore I = (1/L) \int_0^{\pi/2} V_m \sin(\omega t) dt$$

1 mark

$$\therefore I = (V_m/\omega L) \sin(\omega t - \pi/2)$$



1 mark

$$\therefore I = I_m \sin(\omega t - \pi/2).$$


1 mark

2 c) R-C Series Circuit:

Circuit 1 mark,

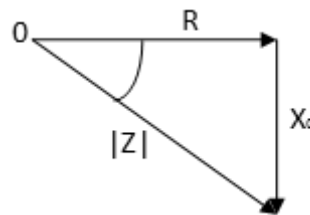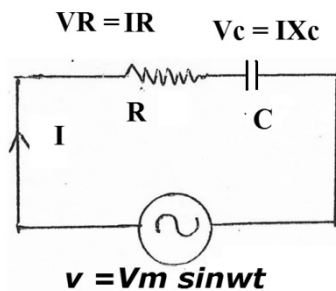

Impedance triangle 1 mark,

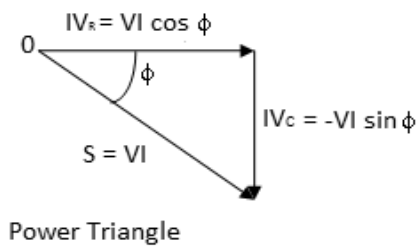

Power triangle 2 marks.



2 d) Formula/Expression for:

1) Active power:  $P = VI \cos\phi$ . (W) 1 mark

2) Reactive power:  $Q = VI \sin \phi$ . (VAR) 1 mark

3) Apparent power:  $S = V I$ . (VA) 1 mark

4)

$$\text{Power Factor} = \frac{\text{Active power (P)}}{\text{Apparent power (S)}} \quad 1 \text{ mark}$$

2 e) i) Given :  $Z = 25 \angle -45^\circ \Omega$

Let us convert it to rectangular form,  $r = 25$  &  $\theta = -45^\circ$

$$\begin{aligned} \text{Its rectangular form is, } Z &= 25 \cos 45^\circ - j 25 \sin 45^\circ \\ &= (17.67 - j 17.67) \text{ ohm} \end{aligned}$$

Comparing it with  $Z = R + j X$

Resistance (R) = 17.67  $\Omega$  and  $X_C = 17.67 \Omega$  1 mark

Taking  $f=50$  Hz,  $X_C = 1/(2\pi f C)$ .

$$C = 1/(2 \pi \times 50 \times ) = 1.800 \times 10^{-4} \text{ F} = 180 \mu\text{F}. \quad 1 \text{ Mark}$$

ii) Given :  $Z = 10 - j15 \Omega$

$\therefore$  Resistance (R) = 10  $\Omega$  and  $X_C = 15\Omega$  1 mark

$X_C = 1/(2\pi f C)$ ,  $C = 1/(2\pi f X_C)$

$$C = 1/(2\pi \times 50 \times 15) = 2.1231 \times 10^{-4} \text{ F} = 212.31 \mu\text{F}. \quad 1 \text{ mark}$$

2 f) Given:  $R = 75 \Omega$ ,  $C = 60 \mu\text{F} = 60 \times 10^{-6} \text{ F}$ , voltage = 230 V,  $f = 50$  Hz

i)  $X_C = 1 / ( 2 \pi f C )$

$$\begin{aligned} &= 1 / ( 2 \times \pi \times 50 \times 60 \times 10^{-6} ) \\ &= 53.05 \Omega \end{aligned}$$

1 mark

ii) Now,  $|Z| = \sqrt{(R^2 + X_C^2)}$

$$= \sqrt{(75^2 + 53.05^2)}$$

$$= \sqrt{(5625 + 2814.3)}$$

$$= 91.87 \Omega$$

$\therefore$  Current = Voltage / Impedance

$$= 230 / 91.87$$

$$= 2.5 \text{ A}. \quad 1 \text{ Mark}$$

iii) Power factor =  $\cos \phi = R / |Z|$

$$= 75 / 91.87$$


$$= 0.816 \text{ lead}. \quad 1 \text{ mark}$$

iv) Active power =  $VI \cos \phi = 230 \times 2.5 \times 0.816$

$$= 469.2 \text{ Watt} \quad 1 \text{ mark}$$



3 a) Resonance in series RLC circuit:

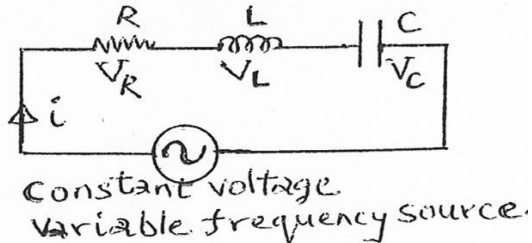


As the frequency is increased from zero towards higher values at a certain frequency  $f_0$ ,  $X_L = X_C$  and the net reactance of the circuit becomes zero. This is resonance condition. At resonance the voltages across the inductive reactance and capacitive reactance ( $X_L$  and  $X_C$ ) are equal and opposite in phase.

$V_L = -V_C$  and hence  $V_L + V_C = 0$ , (phasor addition).

1 mark

Also  $Z = \sqrt{R^2 + (X_L - X_C)^2}$  and  $V = \sqrt{V_R^2 + (V_L - V_C)^2}$

Give  $V = V_R$ .

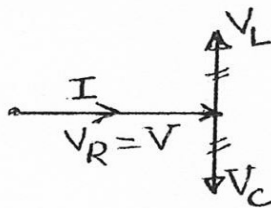

1 mark

Hence the supply voltage applied is across the resistance  $R$ ,  $V = V_R$ .

The impedance is minimum at resonance.


Current is max. =  $I_0 = V/R$ . And is in phase with applied voltage.

As  $X_L = X_C$ , we have  $2\pi f_0 L = 1/(2\pi f_0 C)$  which gives us

$f_0 = 1/[2\pi\sqrt{LC}]$ . (Where  $L$  = coefficient of inductance in henry, and  $C$  =

1 mark

Capacitance in farads).

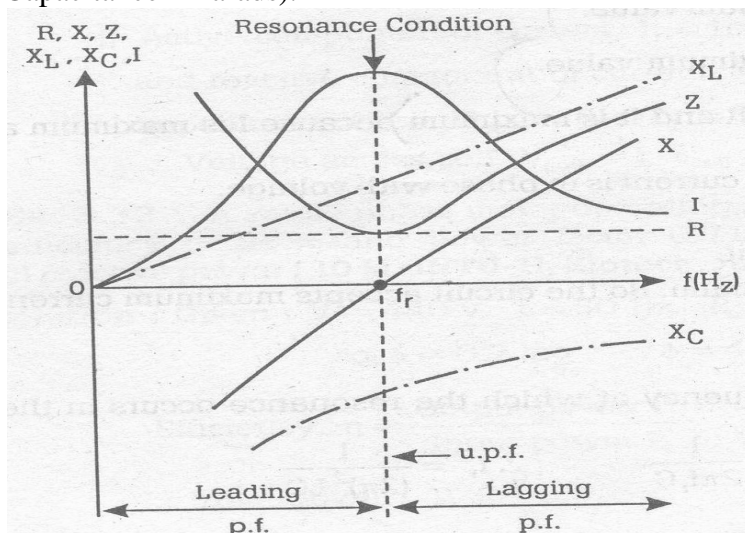

1 mark



**Summer – 2014 Examinations**

**Subject Code : 17323 (ECN)**

**Model Answer**

**Page No : 8 of 23**

3 b) Compare series and parallel resonant circuits: (any four points)

	<u>Parameter</u>	<u>Series resonant circuit</u>	<u>Parallel resonant ckt</u>
1	Impedance	minimum = R	maximum = L/(CR)
2	Current	maximum= V/R	minimum = V/(L/CR)
3	Resonant frequency	$f_r=1/[2\pi\sqrt{LC}]$	$f_r=(1/2\pi)\sqrt{\{[1/(LC)]-(R^2/L^2)\}}$
4	Power factor	Unity	unity
5	Magnification	Voltage	current
6	Q	$(1/R)[1/\sqrt{LC}]$	$(1/R)[1/\sqrt{LC}]$

1 mark  
each point  
any four =  
4 marks

3 c) Impedance  $Z_1 = (8+j6) \Omega = 10 \angle 36.87^\circ$ , Impedance  $Z_2 = (4+j4) \Omega = 5.66 \angle 45^\circ$

i) Branch Current  $(i_1) = V/Z_1$

$$= 200 \angle 0^\circ / 10 \angle 36.87^\circ$$

$$= 20 \angle -36.87^\circ \text{ A}$$

1 mark

ii) Branch Current  $(i_2) = V/Z_2$

$$= 200 \angle 0^\circ / 5.66 \angle 45^\circ$$

$$= 35.34 \angle -45^\circ \text{ A}$$

1 Mark

iii) Total Impedance  $Z_T = (Z_1 * Z_2) / (Z_1 + Z_2)$

$$= (10 \angle 36.87^\circ * 5.66 * \angle 45^\circ) / ((8 + j6) + (4 + j4))$$

$$= 56.6 \angle 81.87^\circ / 15.62 \angle 39.81^\circ$$

$$= 3.62 \angle 42.06 \text{ ohm}$$


Total Current  $i_T = V / Z_T$

$$= 200 \angle 0^\circ / 3.62 \angle 42.06^\circ$$

$$= 55.25 \angle -42.06^\circ \text{ A}$$

1 mark

Phasor Diagram

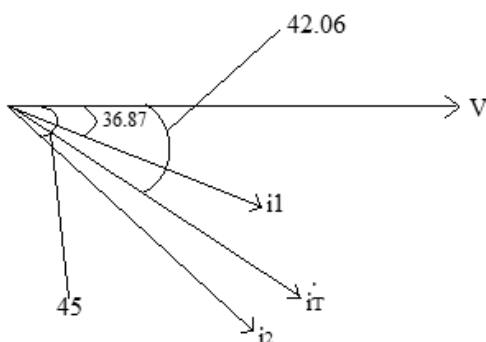

1 mark





3 d) Given :  $R = 100 \Omega$  ,  $L = 0.2 \text{ H}$  ,  $C = 150 \mu\text{F}$  ,  $V = 230 \text{ V}$  ,  $f = 50 \text{ Hz}$ .

Soln :  $X_L = 2\pi fL$

$$= 2\pi * 50 * 0.2$$

$$= 62.8 \Omega$$

$$X_C = 1 / 2\pi fC$$

$$= 2\pi * 50 * 150 * 10^{-6}$$

$$= 1 / 47100 * 10^{-6}$$

$$= 21.23 \Omega$$

$$Z = \sqrt{[R^2 + (X_L - X_C)^2]}$$

$$= \sqrt{[100^2 + (62.8 - 21.23)^2]}$$

$$= \sqrt{[10000 + 1728.06]}$$

$$= 108.29 \Omega$$

Now,  $I = V / Z$

$$= 230 / 108.29$$

$$= 2.12 \text{ A}$$

1 mark

Power factor =  $\cos \Phi = R / Z$

$$= 100 / 108.29$$

$$= 0.923 \text{ (lag)}$$

1 Mark

Power factor is lagging because  $X_L > X_C$

1 mark

Power consumed by ckt =  $VI \cos \Phi = 230 * 2.12 * 0.923 = 450 \text{ Watt}$

1 mark

3 e) i) Taking  $i_2$  as reference phasor,  
 $i_3$  is leading current  
and  $i_1$  is lagging current.

1 mark

1 mark

ii)  $i_1$  lags behind  $i_3$  by  $(40+30) = 70^\circ$

2 marks

3 f) Given :

$V_L = 146.2 \text{ volt}$  ,  $V_R = 150 \text{ volt}$  , supply voltage  $V = 220 \text{ volt}$  ,  $f = 50\text{Hz}$  ,  $I = 10\text{A}$ .

Sol<sup>n</sup>: Total impedance of coil =  $Z = V / I = 220 / 10 = 22 \Omega$

Series resistance  $R = V_R / I = 150 / 10 = 15 \Omega$

Now, total  $|Z| = \sqrt{[(R + R_L)^2 + X_L^2]}$ ,

$R_L$  &  $X_L$  = resistance & reactance of coil respectively,

$$|Z|^2 = (R + R_L)^2 + X_L^2$$

$$\therefore 22^2 = (15 + R_L)^2 + X_L^2$$

$$\therefore 484 = 225 + 30R_L + R_L^2 + X_L^2$$

But,  $R_L^2 + X_L^2 = Z_L^2$  where  $Z_L$  is impedance of coil

$$\therefore 484 = 225 + 30R_L + Z_L^2$$

$$\therefore 259 = 30R_L + Z_L^2$$

But,  $Z_L = V_L / I$

$$= 146.2 / 10$$

$$= 14.62 \Omega$$



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION  
(Autonomous)  
(ISO/IEC-27001-2005 Certified)

Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer

Page No : 10 of 23

$$259 = 30R_L + (14.62)^2$$
$$30R_L = 45.2556$$

i)  $R_L = 1.51 \Omega$  1 Mark

Now,

$$X_L = \sqrt{(Z_L^2 - R_L^2)}$$
$$= \sqrt{[(14.62)^2 - (1.51)^2]}$$
$$= \sqrt{(213.74 - 2.28)}$$
$$= 14.54 \Omega$$

Now,

ii) Inductance of coil,  $L = X_L / (2\pi f) = 14.54 / (2\pi * 50)$   
 $= 0.0463 \text{ H}$  1 Mark

iii) Power consumed by coil,  $P_L = I^2 * R_L$   
 $= 10^2 * 1.51$   
 $= 151 \text{ watt}$  1 Mark

iv) P.F. of total circuit  $= R / Z$   
 $= 15 / 22$   
 $= 0.68 \text{ (lag)}$  1 Mark

4 a) Compare three phase system with single phase system (4 points)

Sr. No.	Parameter	Single Phase System	Three Phase System
1	Line Voltage	Low(230)	High(415V)
2	Transmission Efficiency	Low	High
3	Size of machine to produce same output	Larger	smaller
4	Cross sectional area of conductors (for equal power)	Larger	smaller
5	Application	Domestic, small power application	Industrial large power applications
6	No. of conductors	Two	Three or four

Any four points  
1 Mark for each point

4 b) Given :  $R = 15\Omega$ ,  $L = 0.03\text{H}$ ,  $V_L = 440\text{V}$ ,  $50 \text{ Hz}$ .

Soln : For delta connected load,

$$V_{ph} = V_L = 440 \text{ V}$$

$$Z_{ph} = R + jX_L$$

$$= 15 + j(2\pi * 50 * 0.03)$$



Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer

Page No : 11 of 23

$$= 15 + j(9.42)$$
$$= 17.713 \angle 32.13^\circ$$

i) Now,  $I_{ph} = V_{ph} / Z_{ph}$

$$= 440 / (17.713 \angle 32.13^\circ)$$
$$= 24.84 \angle -32.13^\circ$$

1 Mark

ii)  $I_L = \sqrt{3} * I_{ph}$

$$= \sqrt{3} * 24.8$$
$$= 42.95 \text{ A}$$


1 Mark

iii) Power consumed =  $P = \sqrt{3} V_L I_L \cos \phi$

$$= \sqrt{3} * 440 * 42.95 * \cos(32.13)$$
$$= 27722 \text{ watt} = 27.722 \text{ kW}$$

1 Mark

iv)

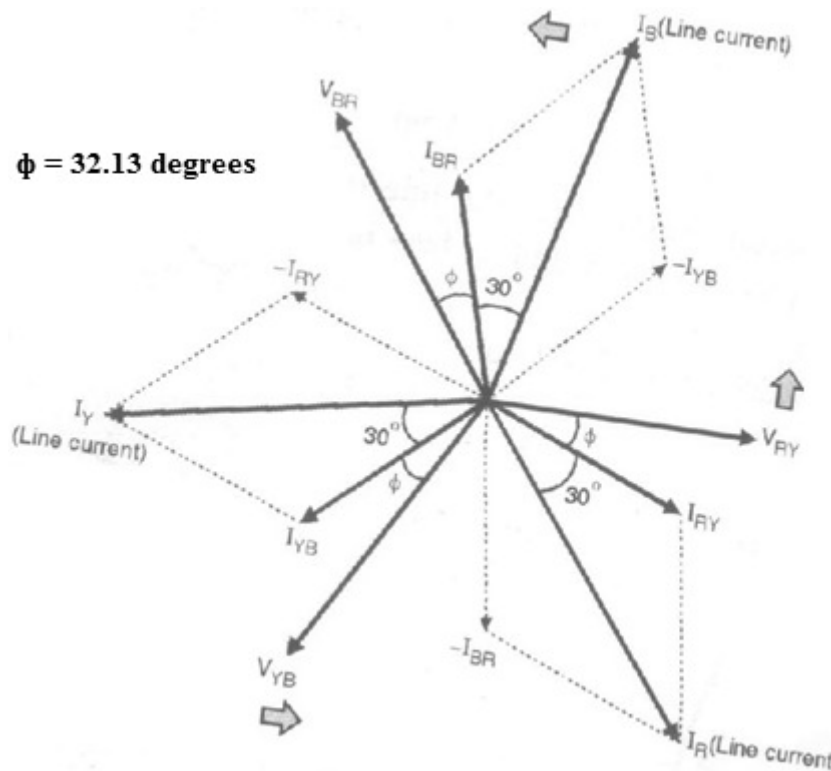

Labeled  
phasor  
diagram

1 Mark



**Summer – 2014 Examinations**

**Subject Code : 17323 (ECN)**

**Model Answer**

**Page No : 12 of 23**

4 c) Given:  $Z_{ph}=(17.32+j10)\Omega$ ,  $3\Phi$ ,  $f=50\text{Hz}$ ,  $V_L=400\text{V}$ , Star connection.

Solution:  $Z_{ph} = \sqrt{(17.32^2 + 10^2)} = \sqrt{(299.98+100)} = 20 \Omega$

$V_{ph} = V_L / \sqrt{3} = 400 / \sqrt{3} = 230.94 \text{ V}$

$I_{ph} = V_{ph} / Z_{ph} = 230.94 / 20 = 11.15 \text{ A}$

1 Mark

Now, i)  $\cos \Phi = R / |Z_{ph}| = 17.32 / 20 = 0.866$

ii) Power consumed =  $3 V_{ph} I_{ph} \cos \Phi = 3 * 230.94 * 11.15 * 0.866 = 6929.79 \text{ W}$

1 Mark

iii) For delta connection,  $V_{ph} = V_L = 400\text{V}$



$I_{ph} = V_{ph} / Z_{ph} = 400 / 20 = 20\text{A}$

1 mark

Power consumed =  $3 V_{ph} I_{ph} \cos \Phi = 3 * 400 * 20 * 0.866 = 20784 \text{ W}$

1 Mark

4 d)

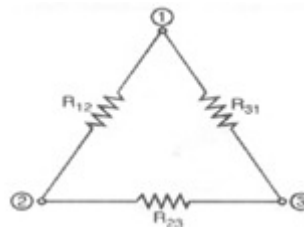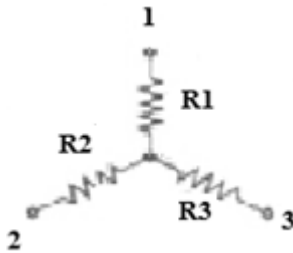

We write expressions for equivalent resistances between corresponding terminals of the two networks and proceed.

Resistance between 1 and 2

for star =  $R_1 + R_2 =$  (for delta) =  $\frac{R_{12} (R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})}$  -----(1)

Resistance between 2 and 3

for star =  $R_2 + R_3 =$  (for delta) =  $\frac{R_{23} (R_{12} + R_{31})}{(R_{12} + R_{23} + R_{31})}$  -----(2)

Resistance between 3 and 1

for star =  $R_3 + R_1 =$  (for delta) =  $\frac{R_{31} (R_{12} + R_{23})}{(R_{12} + R_{23} + R_{31})}$  -----(3)

1 mark

Subtracting (2) from (3) we get,



Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer

Page No : 13 of 23

$$R_1 - R_2 = \frac{R_{12}(R_{31} - R_{23})}{(R_{12} + R_{23} + R_{31})} \quad \text{-----(4)}$$

Adding (1) and (4) and simplifying we get

$$2R_1 = \frac{2R_{12}R_{31}}{(R_{12} + R_{23} + R_{31})}, \text{ hence } R_1 = \frac{R_{12}R_{31}}{(R_{12} + R_{23} + R_{31})} \quad \text{1 mark}$$

$$\text{Similarly } R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}} \quad R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{-----(5)}$$

From above expressions

$$\frac{R_1}{R_2} = \frac{R_{31}}{R_{23}}, \quad \frac{R_2}{R_3} = \frac{R_{12}}{R_{31}} \text{ and } \frac{R_3}{R_1} = \frac{R_{23}}{R_{12}} \quad \text{-----(6)} \quad \text{1 mark}$$

$$\text{From (5) } R_{12} = [R_1(R_{12} + R_{23} + R_{31})/R_{31}]$$


$$= R_1 \left( \frac{R_{12}}{R_{31}} + \frac{R_{23}}{R_{31}} + 1 \right) \quad \text{1 mark}$$

$$\text{Using (6) } R_{12} = R_1 \left( \frac{R_2}{R_3} + \frac{R_2}{R_1} + 1 \right) = \left( \frac{R_1 R_2}{R_3} + R_2 + R_1 \right).$$

Similarly we can write,

$$R_{23} = \left( \frac{R_3 R_2}{R_1} + R_2 + R_3 \right) \quad \text{and} \quad R_{31} = \left( \frac{R_3 R_1}{R_2} + R_3 + R_1 \right)$$

4 e) Given circuit is

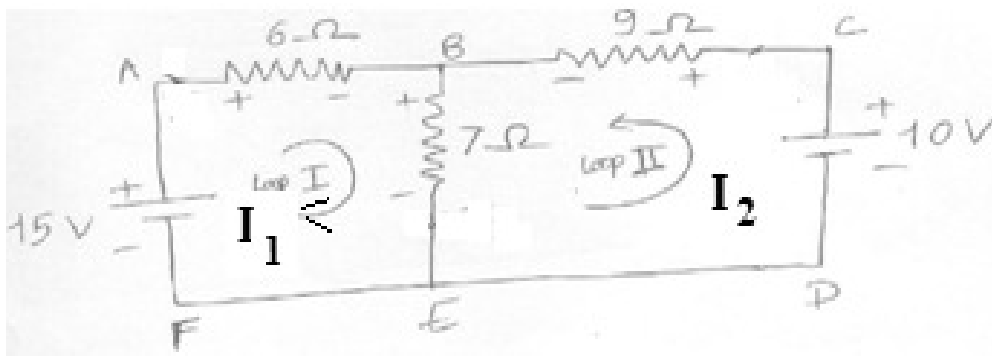

In loop ABEFA by KVL,



**Summer – 2014 Examinations**

**Subject Code : 17323 (ECN)**

**Model Answer**

**Page No : 14 of 23**

$$13I_1 + 7I_2 = 15 \dots\dots\dots(1)$$

Equations

In loop CBEDC by KVL,

1 and 2 =

$$7I_1 + 16I_2 = 10 \dots\dots\dots (2)$$

1 Mark,

Solving equations (1) & (2) we get

$$I_2 = 0.157 \text{ A}$$

$$I_1 = 1.07 \text{ A}$$

1 mark


∴ current through 7Ω resistance is  $I_1 + I_2 = 1.227 \text{ A}$ .

1 Mark

1 mark

4 f) Given Circuit is

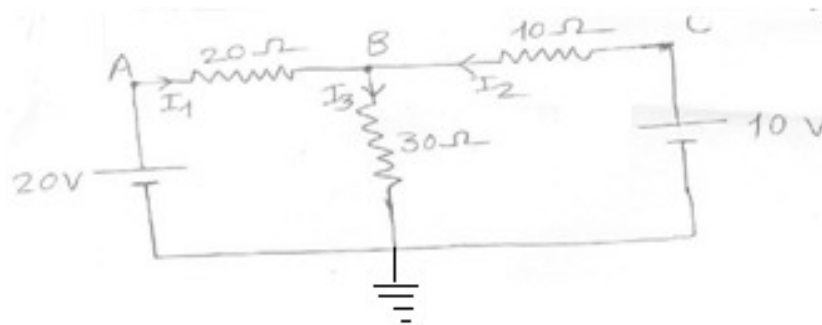Students may determine current in any one of the three resistances to which marks will be awarded as given



Apply KCL at node B,  $I_3 = I_1 + I_2$

But,  $I_1 = (V_A - V_B) / 20$ ,  $I_2 = (V_C - V_B) / 10$  &  $I_3 = V_B / 30$

$$V_B / 30 = [(20 - V_B) / 20] + [(V_C - V_B) / 10]$$

1 Mark

But,  $V_A = 20\text{V}$  and  $V_C = 10\text{V}$

$$V_B / 30 = [(20 - V_B) / 20] + [(10 - V_B) / 10]$$

$$2V_B = 3(20 - V_B) + 6(10 - V_B)$$

$$2V_B = 60 - 3V_B + 60 - 6V_B$$

$$11V_B = 120$$

$$V_B = 10.91 \text{ V}$$

1 Mark

• Current in 10Ω resistance is,

$$I_2 = (V_C - V_B) / 10$$

$$= (10 - 10.91) / 10$$

$$= -0.091\text{A}$$

2 Marks

Negative sign indicates that the actual direction of this current is opposite to that we assumed. OR



Summer – 2014 Examinations

Subject Code : 17323 (ECN)


Model Answer

Page No : 15 of 23

- Current in 30 ohm =  $I_3 = V_B/30 = 10.91/30 = 0.3636$  A. OR 2 marks
- Current in 20 ohm =  $I_1 = (20-10.91)/20 = 0.4545$  A. 2 marks

5 Attempt any two 16 marks

5 a)

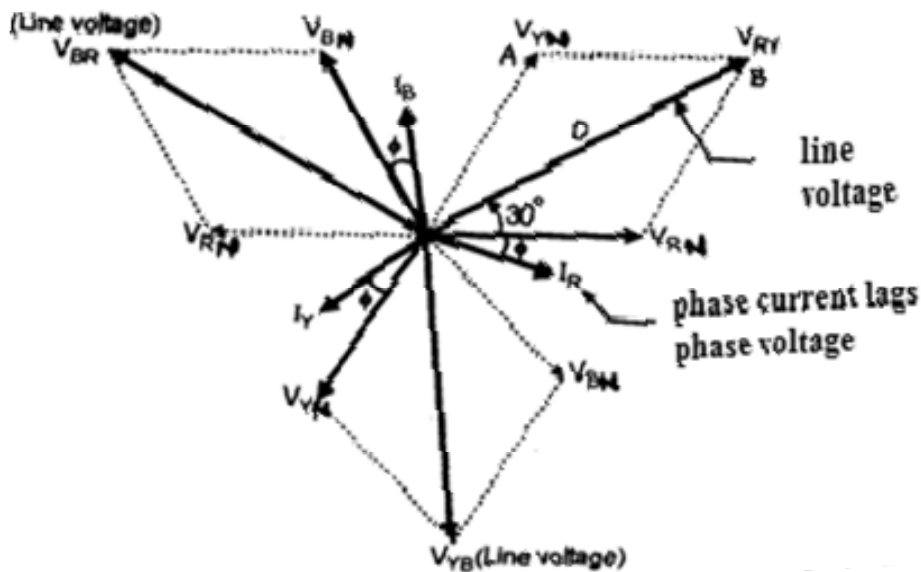

Labeled  
phasor  
diagram  
2 Marks

$$\text{Let } V_R = V_{m(\text{ph})} \sin \omega t$$

Where  $V_{m(\text{ph})}$  denotes the peak phase voltage.

$$\text{Hence } V_Y = V_{m(\text{ph})} \sin (\omega t - 120^\circ)$$

1 Mark

Convert  $V_R$  and  $V_Y$  into their rectangular form to get,

$$V_R = V_m + j0$$

$$\text{And } V_Y = (V_m \cos 120^\circ - j V_m \sin 120^\circ)$$

$$= -0.5 V_m - j 0.866 V_m$$

1 Mark

$$V_{RY} = V_m + j0 - (-0.5 V_m - j 0.866 V_m)$$

$$= (1.5 V_m + j 0.866 V_m) \text{ volts}$$

1 Mark

Converting into polar form we get.

$$V_{RY} = \sqrt{3} V_{m(\text{ph})} \angle 30^\circ \text{ volts}$$

1 Mark

The current passing through any branch of the star connected load is called as the phase current. The current passing through any line R, Y, B is called as the line current.

1 Mark



**Summer – 2014 Examinations**

**Subject Code : 17323 (ECN)**

**Model Answer**

**Page No : 16 of 23**

As current flowing through each line is equal to the current flowing through the corresponding branch, the line current is equal to the phase current.

**∴ For Star Connected Load  $I_L = I_{ph}$**


1 Mark

5 b) Statement of superposition theorem :

The superposition theorem states that, in any linear network containing two or more sources, the response (current) in any element is equal to the algebraic sum of currents caused by individual source acting alone, while other sources are removed with only their internal resistances in place.

3 Marks

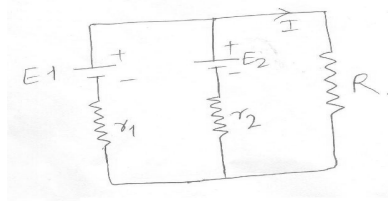Procedural steps to find current in given circuit :



Step 1: Remove  $E_2$  and keep only its internal resistance  $r_2$  in circuit.



Using any relevant method determine  $I'$  as follows;


$$I_1 = E_1 / [r_1 + r_2 R / (r_2 + R)] \text{ and}$$

1 mark

$$I' = I_1 r_2 / [r_2 + R].$$

1 mark

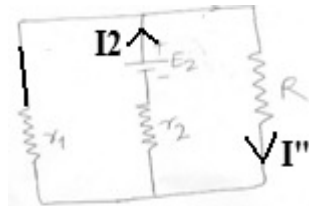Step 2: Remove  $E_1$  and keep only its internal resistance  $r_1$  in circuit.



Using any relevant method determine  $I''$  as follows;

$$I_2 = E_2 / [r_2 + r_1 R / (r_1 + R)] \text{ and}$$

1 mark

$$I'' = I_2 r_1 / [r_1 + R].$$

1 mark

Step 3: Add algebraically the branch currents obtained due to individual sources to





Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer

Page No : 17 of 23

obtain combined effect of the both sources  $I = I' + I''$ .

1 mark

5 c) Statement of Norton's theorem :

It states that, any linear, active, resistive network containing one or more voltage and/or current source can be replaced by any equivalent circuit containing a single current source and equivalent conductance (resistance across the current source).

1 mark


The equivalent current source (Norton's source)  $I_N$  = the short circuit current through the terminals of the load.

The equivalent conductance  $G_N$  (or  $R_N$ ) is the conductance (or resistance) seen between the load terminals with the load removed and sources replaced by their internal resistances.

If  $R_L$  is load resistance then current through it is  $I_L = I_N R_N / (R_N + R_L)$ .


1 mark

Given circuit is,

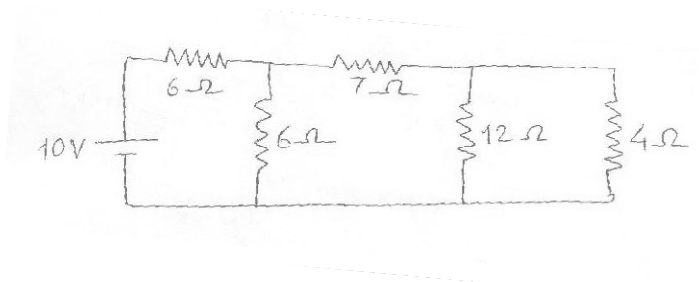


Part I) to obtain value of  $I_N = I_{sc}$  :

Let us short circuit the 4Ω resistance.

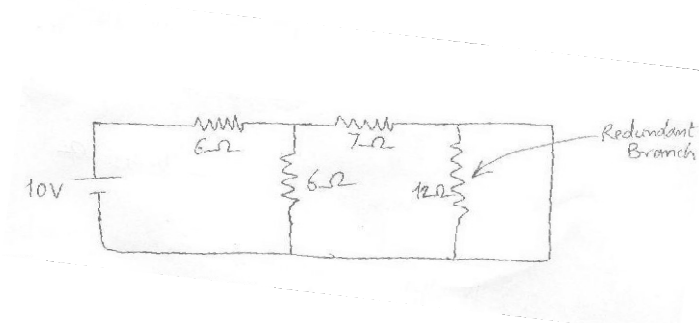

1 Mark

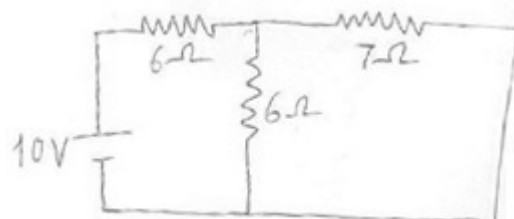Due to redundant branch, circuit reduces to,



$$R_T = [(6 \cdot 7) / (6 + 7)] + 6$$

$$\therefore R_T = 9.23 \Omega$$



**MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION**  
(Autonomous)  
(ISO/IEC-27001-2005 Certified)

**Summer – 2014 Examinations**

**Subject Code : 17323 (ECN)**


**Model Answer**

**Page No : 18 of 23**

$$\begin{aligned} \therefore I_T &= 10 / 9.23 \\ &= 1.0834 \text{ A} \\ \therefore I_N = I_{sc} &= (6 / (6+7)) * 1.0834 \\ &= 0.5 \text{ A} \end{aligned}$$

1 Mark

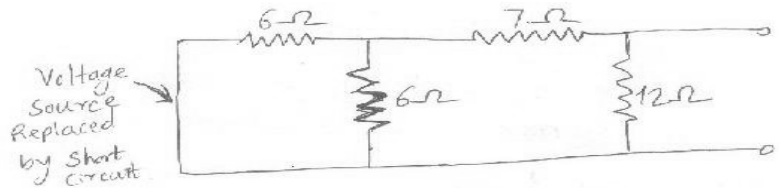Part II) To obtain value of  $R_N$  or  $R_{TH}$



1 Mark


Two  $6\Omega$  resistance are in parallel,  
Their equivalent is  $R_1 = (6 * 6) / (6 + 6)$   
 $= 3\Omega$

$7\Omega$  resistance is in series with  $R_1$

$$\begin{aligned} \therefore \text{their equivalent is,} \\ R_{Th} &= (10 * 12) / (10 + 12) \\ &= 5.45\Omega \end{aligned}$$

1 Mark

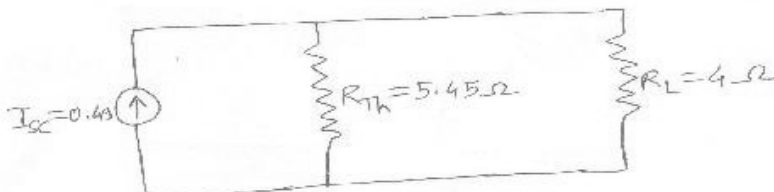Part III) Norton's equivalent circuit can be drawn as,



1 Mark

By current division rule, current through  $4\Omega$  resistance is given


$$\begin{aligned} I_L &= [5.45 / (5.45 + 4)] * 0.5 \\ &= 0.288 \text{ A} \end{aligned}$$

1 Mark

6 Attempt any four.

16 marks

6 a) Given circuit is,

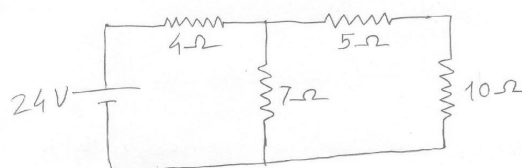

Part 1) Find  $V_{oc}$ :




Summer – 2014 Examinations


Subject Code : 17323 (ECN)

Model Answer

Page No : 19 of 23

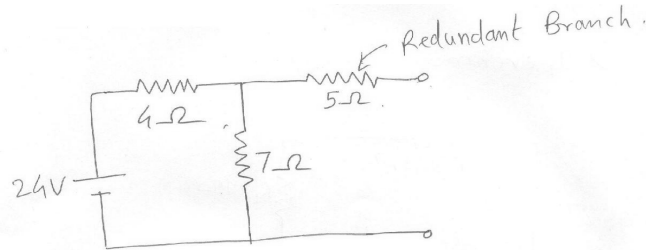

∴ circuit reduces to,

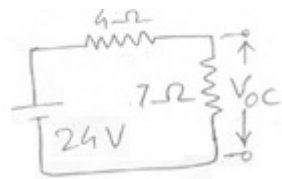


∴ By voltage division rule,

$$V_{OC} = V_{TH} = 24 \times 7 / (7+4) \\ = 15.27 \text{ V}$$

1 Mark

Part 2) Find  $R_{TH}$

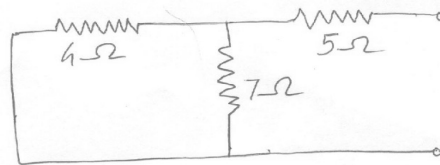

$4\Omega$  and  $7\Omega$  resistances are in parallel,  
Their equivalent is,


$$R_P = (4 * 7) / (4 + 7) \\ = 2.545\Omega$$

$5\Omega$  resistance is in series with this combination,

$$\therefore R_{TH} = 5 + 2.545 \\ = 7.545\Omega$$

1 Mark

Part 3) Application:

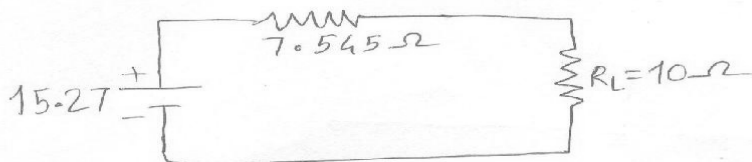


1 Mark

$$\therefore I_L = V / R_{Total} \\ = 15.27 / (7.545 + 10) \\ = 15.27 / 17.545 \\ = 0.87 \text{ A}$$


1 Mark



6 b)

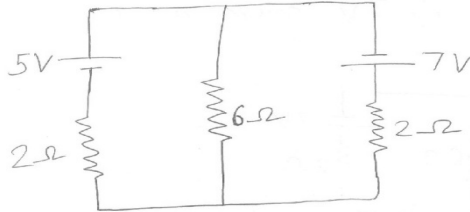

Step 1) Using 5 V source only,

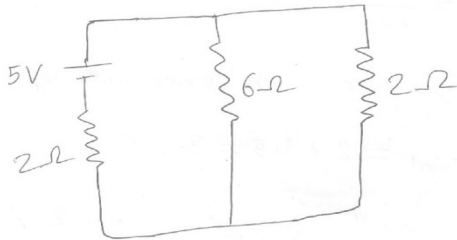

6Ω & 2Ω resistance are in parallel,

$$\therefore R_P = (6 \times 2) / (6 + 2) \\ = 1.5\Omega$$

2Ω resistance is in series with  $R_P$ ,

$$\therefore R_{\text{Total}} = 2 + 1.5 \\ = 3.5\Omega$$

$\therefore$  Total current is,


$$I_T = V / R_{\text{Total}} \\ = 5 / 3.5 \\ = 1.428 \text{ A}$$

By current division rule, current through 6Ω is,

$$I_L' = [2 / (2+6)] * 1.428 \\ = 0.357 \text{ A}$$

1 Mark

Step 2): Keeping only 7 V source,

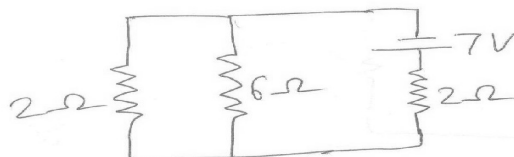

2Ω and 6Ω resistance are in parallel.

$$\therefore R_P = (6 \times 2) / (6 + 2) \\ = 1.5\Omega$$

2Ω resistance is in series with  $R_P$

$$\therefore R_{\text{Total}} = 2 + 1.5 \\ = 3.5\Omega$$

$$\therefore \text{Total current} = V / R_{\text{Total}}$$



Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer

Page No : 21 of 23

$$= 7 / 3.5$$
$$= 2A$$

By current division rule, current through  $6\Omega$  resistance is,

$$I'_L = [2 / (2+6)] * I_{Total}$$
$$= (2 / 8) * 2$$
$$= 0.5 A$$


1 Mark

Step 3): Total current through  $6\Omega$  resistance, according to superposition theorem is,

$$I_L = I'_L + I''_L$$
$$= 0.357 + 0.5$$
$$= 0.857A$$

2 Marks

6 c)

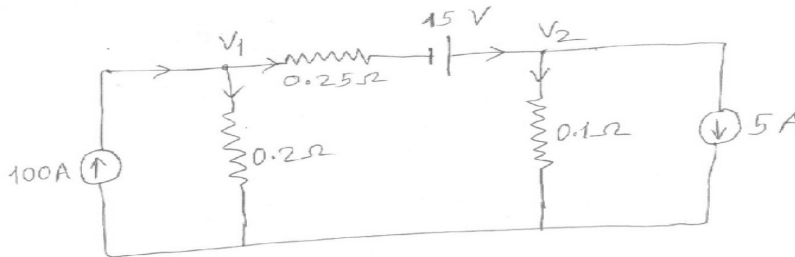

By KCL at node  $V_1$ ,

$$100 = (V_1 / 0.2) + [(V_1 + 15 - V_2) / 0.25]$$
$$100 = 5V_1 + 4(V_1 + 15 - V_2)$$
$$100 = 5V_1 + 4V_1 + 60 - 4V_2$$
$$\therefore 9V_1 - 4V_2 = 40 \quad \text{----- Eq.1}$$

1 Mark

By KCL at node  $V_2$ ,

$$(V_1 + 15 - V_2) / 0.25 = (V_2 / 0.1) + 5$$
$$4(V_1 + 15 - V_2) = 10V_2 + 5$$
$$\therefore 4V_1 + 60 - 4V_2 - 10V_2 = 5$$
$$\therefore 4V_1 - 14V_2 = -55 \quad \text{-----Eq.2}$$

1 Mark

Solving eqns 1 and 2,

$$V_1 = 7.09 V$$

1 Mark

$$V_2 = 5.95 V$$

1 Mark




Summer – 2014 Examinations

Subject Code : 17323 (ECN)

Model Answer


Page No : 22 of 23

6 d) For RC series circuit :

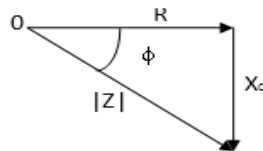

Labeled  
2 Marks

Impedance Triangle

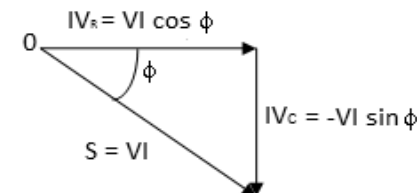

Labeled  
2 Marks

Power Triangle

6 e) The initial and final conditions given are for switching constant direct supplies to the elements (resistor and inductor).

**For Resistor**

**Initial condition:**

According to ohm's law; the relationship between voltage and current, is given by,

$$v = i.R$$

This equation is time independent equation as R is a constant. Thus the current changes instantaneously as soon as the voltage changes or vice versa. That means initial condition at time  $t = 0$  is same as that exists then. Hence if at  $t = 0$  voltage  $v$  is applied the initial current will be  $v/R$  at  $t = 0^+$ .

1 Mark

**Final Condition:**

As ratio of voltage to current is a constant ( $= R$ ) at  $t = \infty$ ; and there is no change in the value of resistor. Hence if at  $t = \infty$ , for voltage existing the current will be  $v/R$  again.

1 Mark

**For Inductor:**

**Initial condition:**

By definition of inductor it opposes any change in current in it, hence for any new circuit conditions imposed on it by switching DC it opposes it and behaves as open circuit for the change (switching). Thus the initial condition in an inductor is same

1 Mark




condition that exists before switching. (that is open circuit for new switching)

Final Condition:

After a long time has elapsed when switching has been done,  $t = \infty$ , Voltage across inductor becomes zero as supply current is constant ( $di = 0$ , from  $V_L = L di/dt$ ). This means it act as short circuit.


1 Mark

6 f)

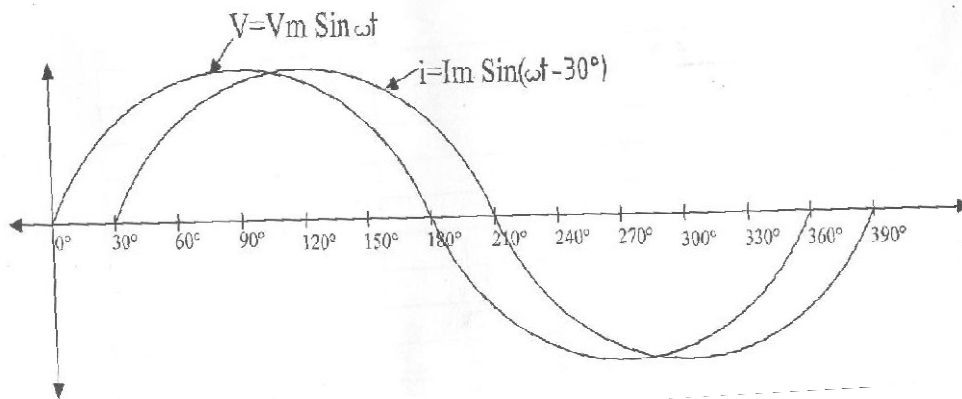

2 Marks

Fig. Waveform when current lags voltage by  $30^\circ$

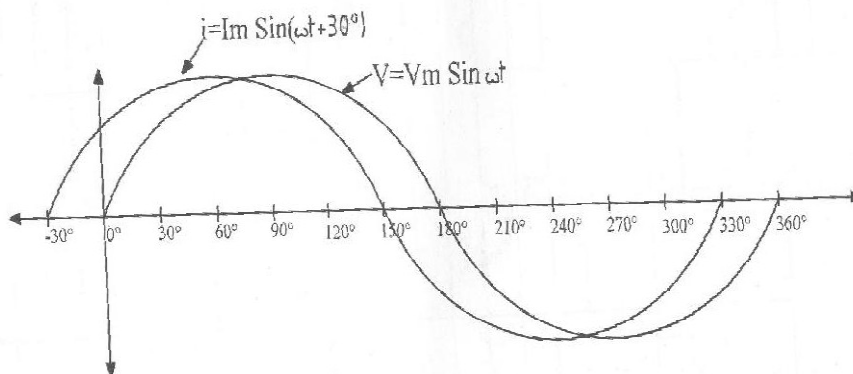

2 Marks

Fig. Waveform when current leads voltage by  $30^\circ$